

Report

Name: Sritharan Reddy Pulicherla

For a full adder with inputs 'a' and 'b' and carry-in as 'cin', The output sum = $a \oplus b \oplus C_{in}$

$$\text{output carry (C-out)} = a \cdot b + (b + a)C_{in}$$

- carry is generated (g) when $a = b = 1$
- carry is propagated (p) when $a + b = 1$

$$\Rightarrow \text{C-out} = g + p C_{in}; \quad g = a \cdot b \quad \text{--- (1)}$$

$$p = a \oplus b \quad \text{--- (2)}$$

For n -bit adder with LSB indexed as 0 and MSB as $n-1$

i th bit accepts C_i as i/p carry and produces C_{i+1} as o/p carry

We can express the o/p of i th stage as.

$$C_{i+1} = G_i + P_i \cdot C_i$$

$$C_{i+1} = G_i + P_i \cdot (G_{i-1} + P_{i-1} \cdot C_{i-1})$$

$$= G_i + P_i \cdot G_{i-1} + P_i \cdot P_{i-1} \cdot C_{i-1}$$

$$\text{let } G_{i,i-1}^2 = G_i + P_i G_{i-1}, \quad P_{i,i-1}^2 = P_i P_{i-1}$$

$$\Rightarrow C_{i+1} = G_{i,i-1}^2 + P_{i,i-1}^2 \cdot C_{i-1}$$

Similarly ^{assuming}

$$G_{i,i-3}^3 = G_{i,i-1}^2 + P_{i,i-1}^2 \cdot G_{i-2,i-3}^2$$

$$P_{i,i-3}^3 = P_{i,i-1}^2 \cdot P_{i-2,i-3}^2$$

$$\Rightarrow C_{i+1} = G_{i,i-3}^3 + P_{i,i-3}^3 C_{i-3}$$

→ assuming unit delay for each computation


computation of $G_{i,i-3}^1$, $G_{i,i-3}^2$, $G_{i,i-3}^3$ takes 1, 2 & 3 unit delays.

Thus computing of final carry-out of 'n' bit adder takes.

'log n' as delay.

We can calculate sum of each stage as $S_i = A_i \oplus b_i \oplus C_i$
 $= P_i \oplus C_i$

Example of a 32-bit Boentkung adder

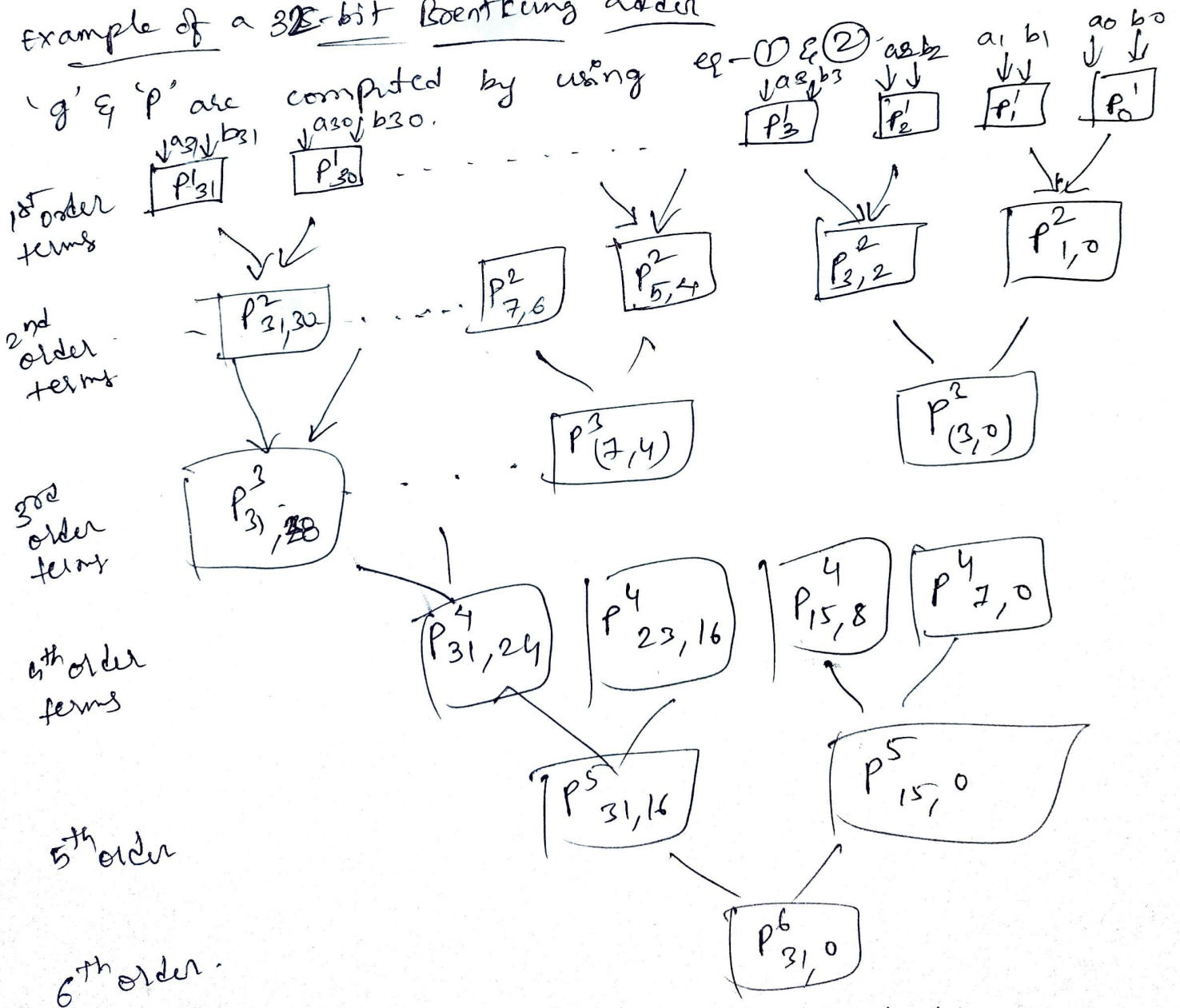

The carry of each stage is computed as

$$c_1 = g_0^1 + p_0^1 c_0, \quad c_2 = \tilde{g}_{1,0}^2 + p_{1,0}^2 c_0$$

$$c_4 = g_{3,0}^3 + p_{3,0}^3 c_0, \quad c_8 = g_{7,0}^4 + p_{7,0}^4 c_0 \quad \text{etc.}$$

References: Prof. Dinesh Sharama lectures - ~~II~~ IIT Bombay